



Labwork - 6#





Name: mohannad alshahrani

Student id: 442100744

1. Introduction

In this lab, the goal was to design and implement different types of digital circuits, specifically focusing on multiplexers 1 to 2 and 2 to 4, decoders, and a full adder. These circuits were drawn in Logisim, and truth tables were created to verify their functionality. By analyzing how different circuits work with various input combinations, I gained a better understanding of how multiplexers select inputs

2. Experiments

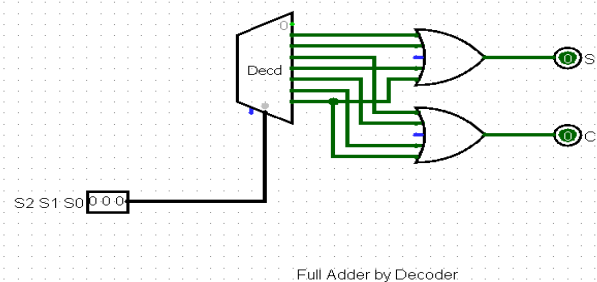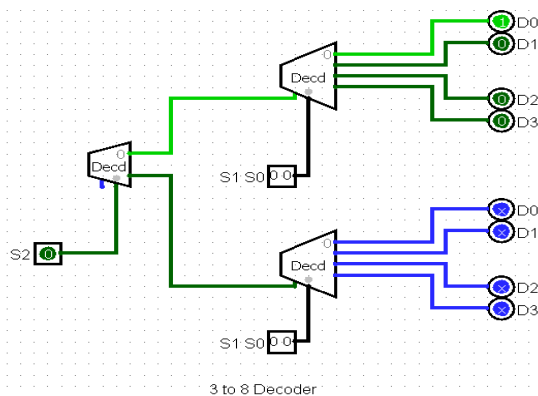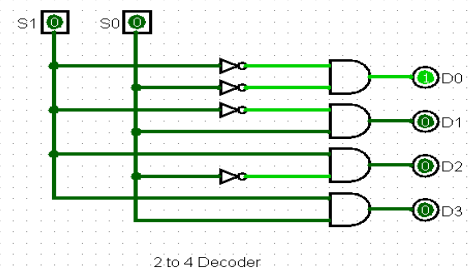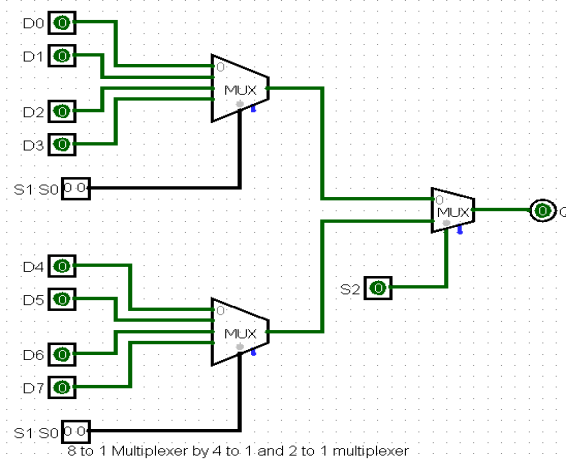

3. Results

You should give the results of each experiment. You may use the truth table to verify the circuits you designed

S2	S1	S0	Q
0	0	0	D0
0	0	1	D1
0	1	0	D2
0	1	1	D3
1	0	0	D4
1	0	1	D5
1	1	0	D6
1	1	1	D7

4. Discussion

Through this lab, I learned how to design and implement multiplexers, decoders, and a full adder using Logisim. Each circuit was tested using truth tables, which helped verify their accuracy. The truth table for the 8-to-1 multiplexer confirmed that the output changed correctly based on the different input combinations of S2, S1, and S0.