

CSC 220
Computer Organization
Final Lab Project


Doctor: MOHAMMAD WAKIL AHMED

Student: Mohannad alshahrani

ID: 442100744

- Introduction:
For this final lab project, I will design and implement an 8-bit Arithmetic Logic Unit with a shifter using Logisim. This project will put in the knowledge and skills I have gained from all the previous labs, including working with combinational and sequential circuits. The goal is to demonstrate my understanding of how to build and simulate a complex digital system.

- Project:

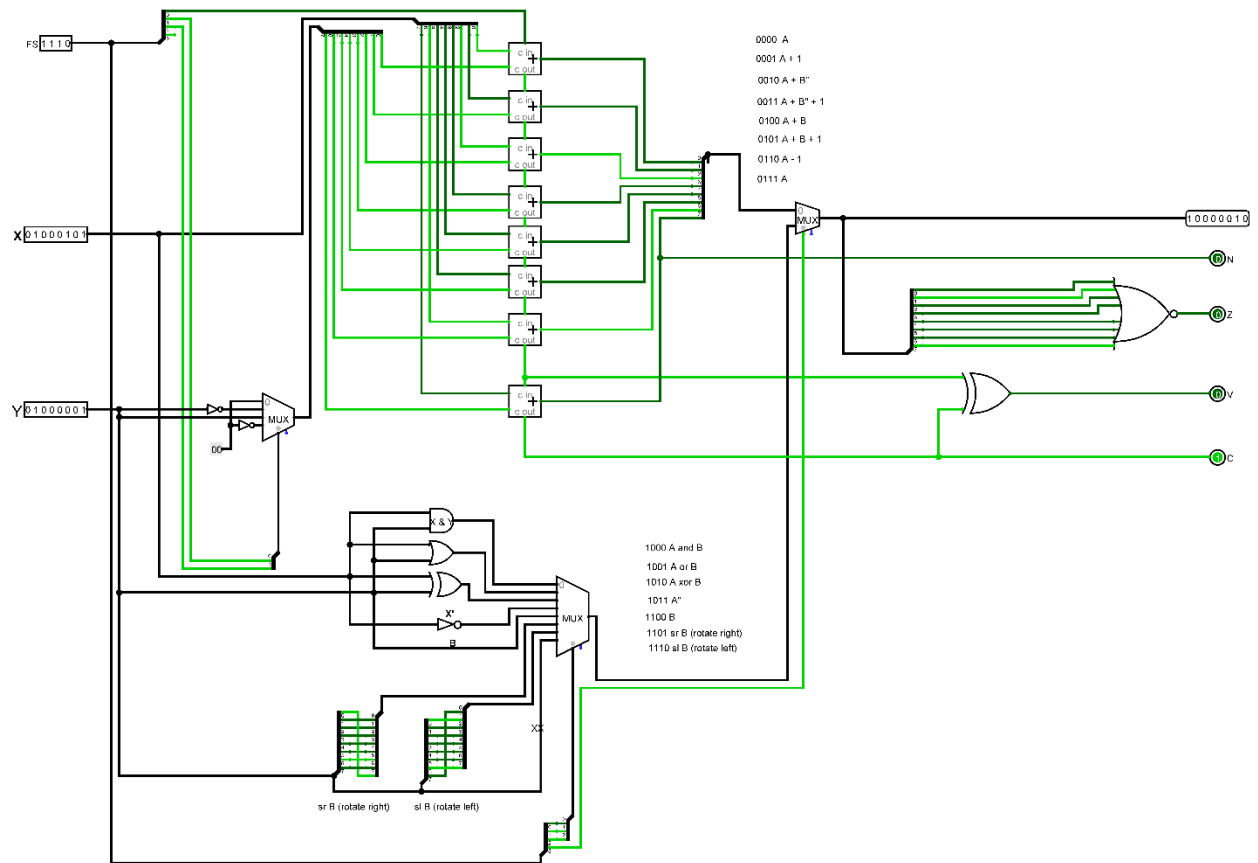

- Test Cases:

S3	S2	S1	S0	Operations	X	Y	F	C	V	N	Z
0	0	0	0	$F = A$	0000 0011	-	0000 0011	0	0	0	0
0	0	0	1	$F = A + 1$	0000 0011	-	0000 0100	0	0	0	0
0	0	1	0	$F = A + B'$	0000 0011	0000 0010	0000 0000	1	0	0	1
0	0	1	1	$F = A + B' + 1$	0000 0011	0000 0010	0000 0001	1	0	0	0
0	1	0	0	$F = A + B$	0000 0011	0000 0010	0000 0101	0	0	0	0
0	1	0	1	$F = A + B + 1$	0000 0011	0000 0010	0000 0110	0	0	0	0
0	1	1	0	$F = A - 1$	0000 0011	-	0000 0001	1	0	0	0
0	1	1	1	$F = A$	0000 0011	-	0000 0011	0	0	0	0
1	0	0	0	$F = A \text{ and } B$	0000 0011	0000 0010	0000 0010	-	-	-	-
1	0	0	1	$F = A \text{ or } B$	0000 0011	0000 0010	0000 0011	-	-	-	-
1	0	1	0	$F = A \text{ xor } B$	0000 0011	0000 0010	0000 0001	-	-	-	-
1	0	1	1	$F = A'$	0000 0011	-	1111 1100	-	-	-	-
1	1	0	0	$F = B$	-	0000 0010	0000 0010	-	-	-	-
1	1	0	1	$F = \text{sr } B$	-	0000 0010	0000 0001	-	-	-	-
1	1	1	0	$F = \text{sl } B$	-	0000 0010	0000 0100	-	-	-	-

Discussion:

with this being our last lab I have gained a lot of experience and now am able to design and illustrate a combination circuit and sequential circuits and also I can arithmetic logic unit and a shifter with help of my professional professor doctor MOHAMMAD WAKIL AHMED.